

Week 9

## Trinity Robotics


10/11/2023


Today's class is about circuits.

We have been working with 1 type, Lets Level Up,  
And expand our knowledge about circuits and learn about  
another way to wire a circuit.

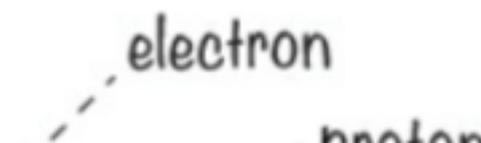Questions:

What (small particles) flows to create electricity?



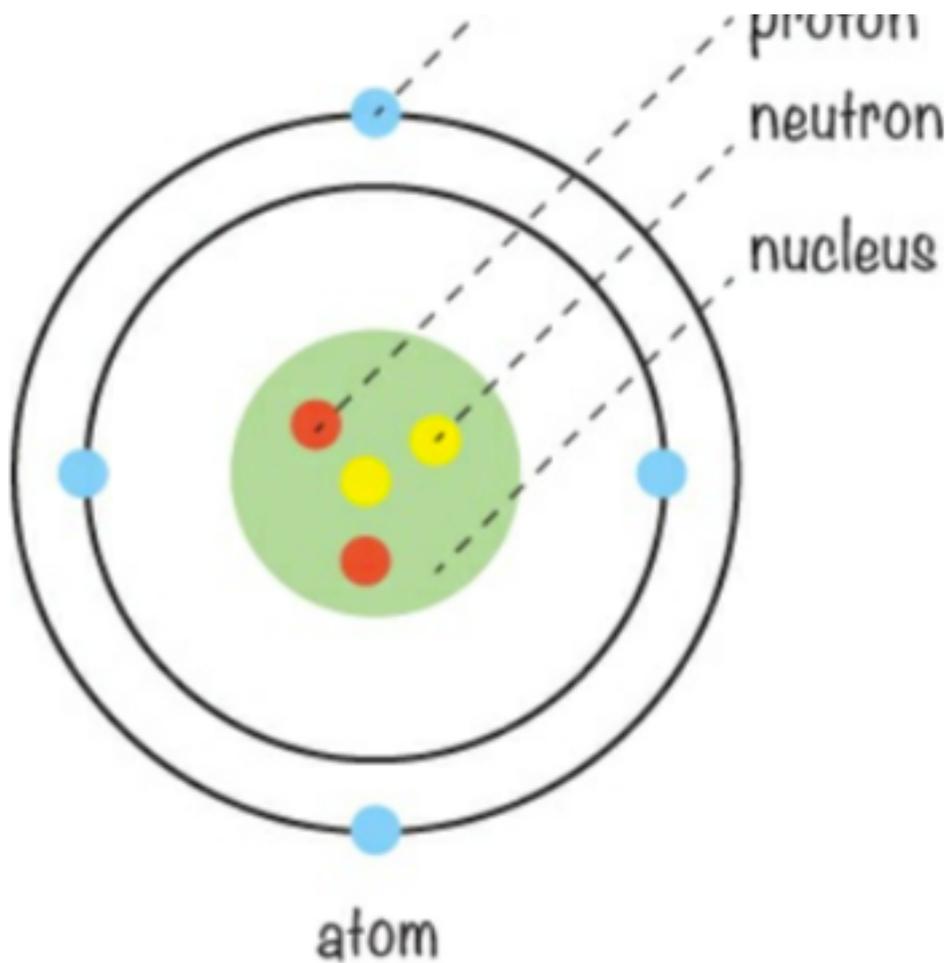

## Series Circuit

Steps:

- (1) Insert batteries, with the switch off (negative terminal is spring)
- (2) Identify your bread board column "a" insert the power supply (red wire) into row 2 of column "a", and the black wire in column 6.
- (3) add a resistor to connect electricity;

connect the resistor from e2 -> t2

(4) insert a LED (light emitted Diode); the positive terminal is the longer leg, insert the LED from


j2 -> j3

(5) find a wire and insert it from i3 -> i6


(6) insert a resistor from f6 -> e6

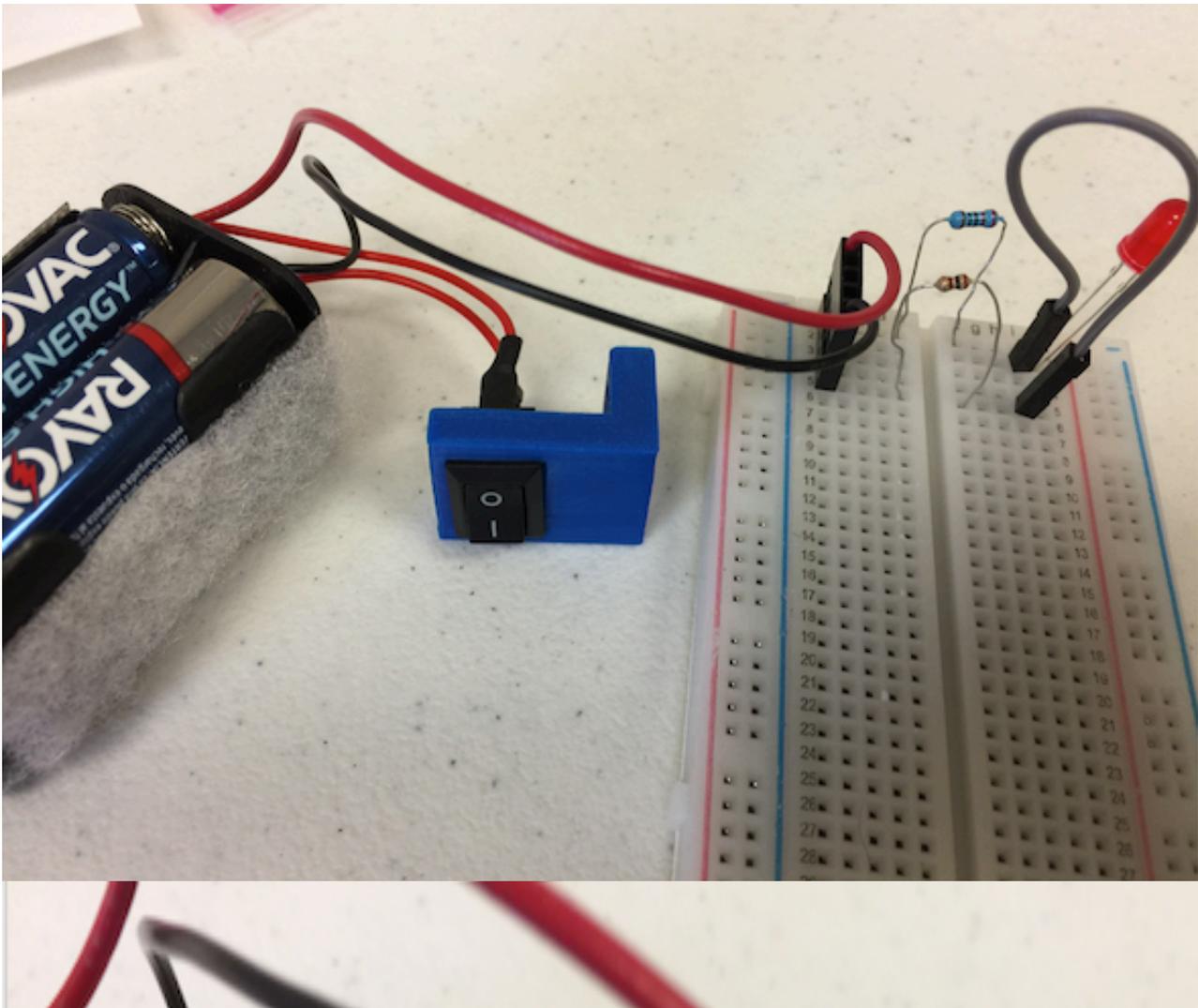(7) review circuit for accuracy, and test. Turn on the switch.

-> reverse the LED... does the LED light up?






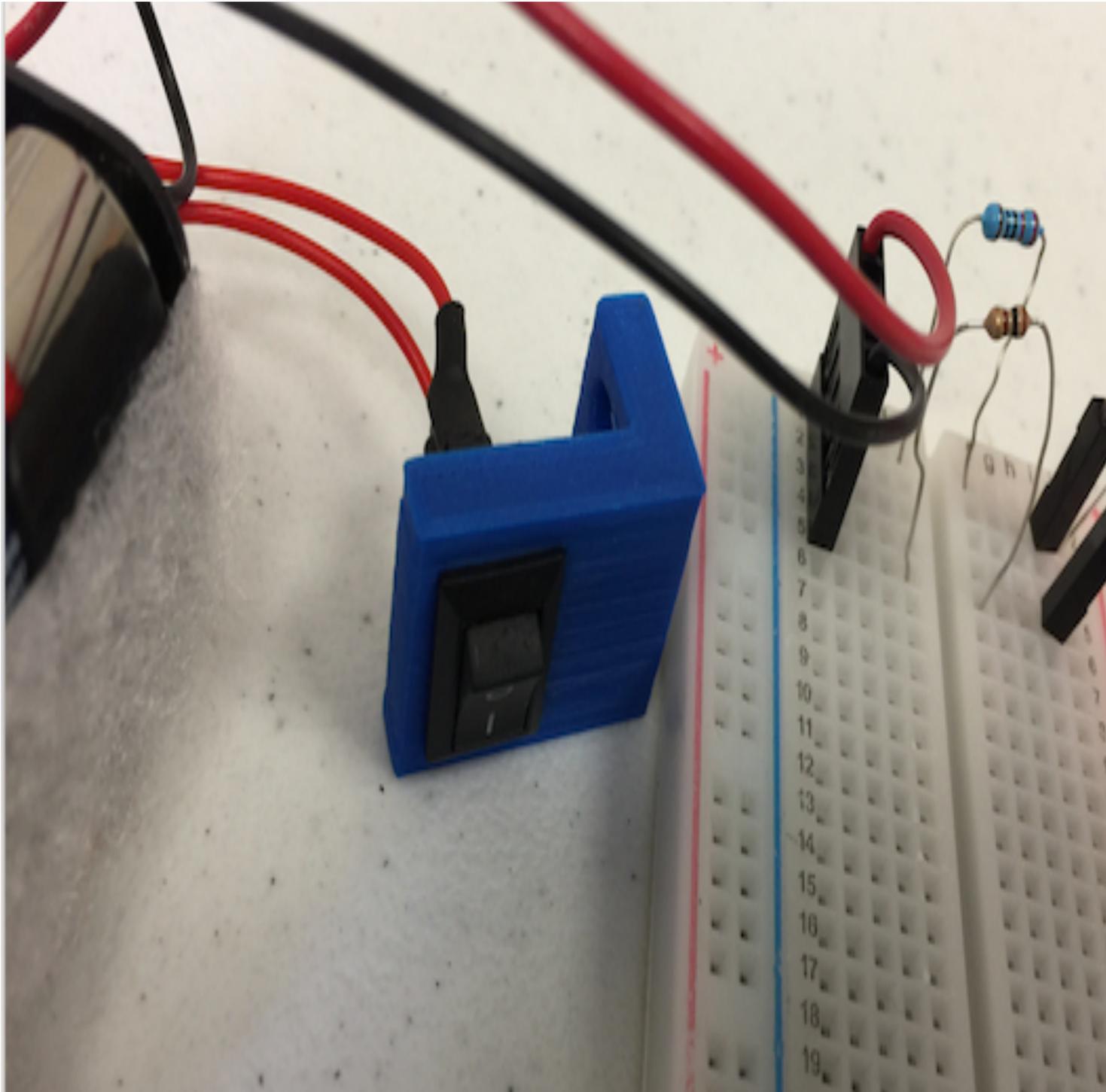

Introduction to Series Vs. Parallel Circuits:

[Series and Parallel Circuits \(Interactive!\): Electronics Basics 5](#)

SERIES

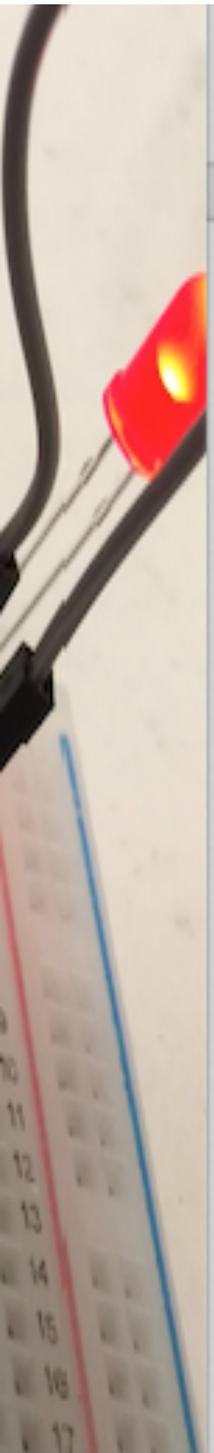



<http://www.youtube.com/watch?v=MMD32gyHVQw>

- Next we will have a hands on Exercise:  
using a 6 volt (4 batteries) power source -
1. Build a series Circuit
  2. Build a Parallel Circuit